



## **ANALOG CIRCUIT DESIGN**

### **PROJECT REPORT**

#### **TOPIC : RC PHASE SHIFT OSCILLATOR**

- **PRESENTED BY:**

|                          |              |
|--------------------------|--------------|
| MR.SIDDHANT GUPTA        | [BT23ECE008] |
| MR.ASHISH PATIL          | [BT23ECE009] |
| MS.AKSHAYA CHANDRASEKHAR | [BT23ECE010] |
| MR.HARISH RAJA           | [BT23ECE011] |
| MR.ADITYA MULAY          | [BT23ECE012] |
| MR.APOORV DESHMUKH       | [BT23ECE013] |

- **PRESENTED TO:**

**DR. PRADNYA GHARE**

Senior Assistant Professor, Department of Electronics and  
Communication Engineering

**DR. ANAMIKA SINGH**

Assistant Professor, Department of Electronics and Communication  
Engineering

**AIM :** IMPLEMENTATION OF RC PHASE SHIFT OSCILLATOR USING OPERATIONAL AMPLIFIER.

**APPARATUS :** OPERATIONAL AMPLIFIER IC741, RESISTOR ( $33\text{K}\Omega \times 2$  ,  $3.6\text{K}\Omega \times 3$  ,  $2\text{M}\Omega$ ), CAPACITORS ( $0.1\mu\text{f} \times 3$ ), CONNECTING WIRES, PERV BOARD, IC HOLDER.

**THEORY :**

An **RC Phase Shift Oscillator** is a **linear oscillator** used to generate **pure sinusoidal waveforms** without requiring any external input signal. It is a **feedback oscillator**, which means it sustains oscillations using energy fed back from its output to its input.

**Detailed Working Mechanism**

**1. Op-Amp as the Active Element:**

- The op-amp is used in **inverting amplifier mode**. It provides a  **$180^\circ$  phase shift** and **amplifies** the signal.
- Its **high input impedance** and **low output impedance** make it ideal for interfacing with the passive RC network.

**2. RC Phase Shift Network:**

- Three RC sections are connected in series.
- Each RC stage contributes a phase shift of  **$60^\circ$**  at the oscillation frequency, adding up to  **$180^\circ$** .
- The network acts as a **frequency-selective feedback path** — it allows a specific frequency (resonant frequency) to pass with correct phase.

**3. Barkhausen Criterion:** For sustained oscillations:

- **Total phase shift** around the loop = 0 degrees OR 360 degrees
- **Loop gain**  $A\beta \geq 1$ 
  - A = amplifier gain
  - $\beta$  = feedback factor (attenuation of RC network)

In this oscillator:

- $A = -R_f/R_1$  (gain of inverting op-amp)

- $B \approx 1/29$ , so  $A \geq 29$

Using complex impedance analysis, each RC section contributes a frequency-dependent phase shift. At a specific frequency:

$$\omega = \frac{1}{RC\sqrt{6}} \Rightarrow f = \frac{1}{2\pi RC\sqrt{6}}$$

This is the frequency at which the total phase shift from the three RC sections becomes exactly  $180^\circ$ , matching the  $180^\circ$  from the op-amp — completing the feedback loop with zero net phase shift.

In practical, if gain is too high, the output amplitude grows uncontrollably; if too low, oscillations die out. To stabilize amplitude:

- **Nonlinear elements** (diodes, FETs) or **automatic gain control** circuits are used in some designs.
- In simple lab setups, we slightly overdesign the gain and allow natural circuit losses to settle the amplitude.

---

### Advantages



- Simple design using basic components.
- Pure sine wave output.
- Good frequency stability for low frequencies (audio range).

### Limitations


- Not suitable for high frequencies (above few hundred kHz) due to RC network loading and op-amp limitations.
- Amplitude can drift if not properly stabilized.
- Requires large gain ( $\geq 29$ ), which might cause distortion if not carefully handled.

## CIRCUIT DIAGRAM:

## MULTISIM SIMULATION

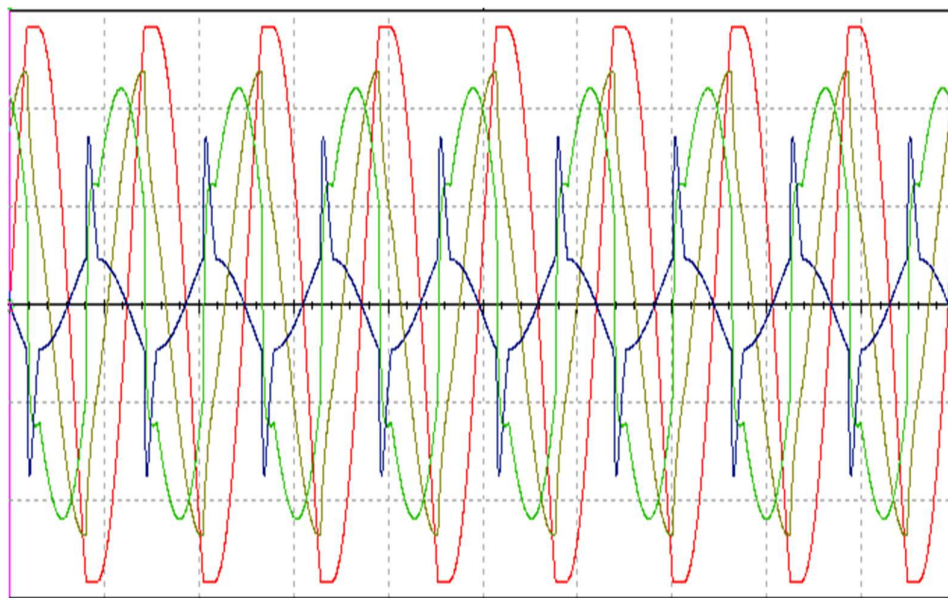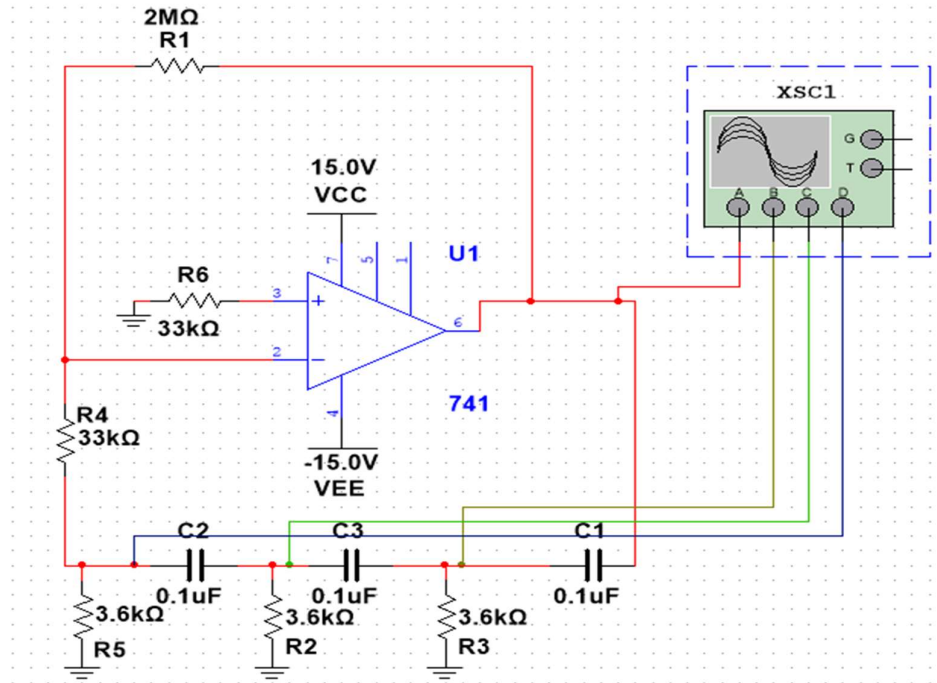

## SOLDERED CIRCUIT ON PERF BOARD

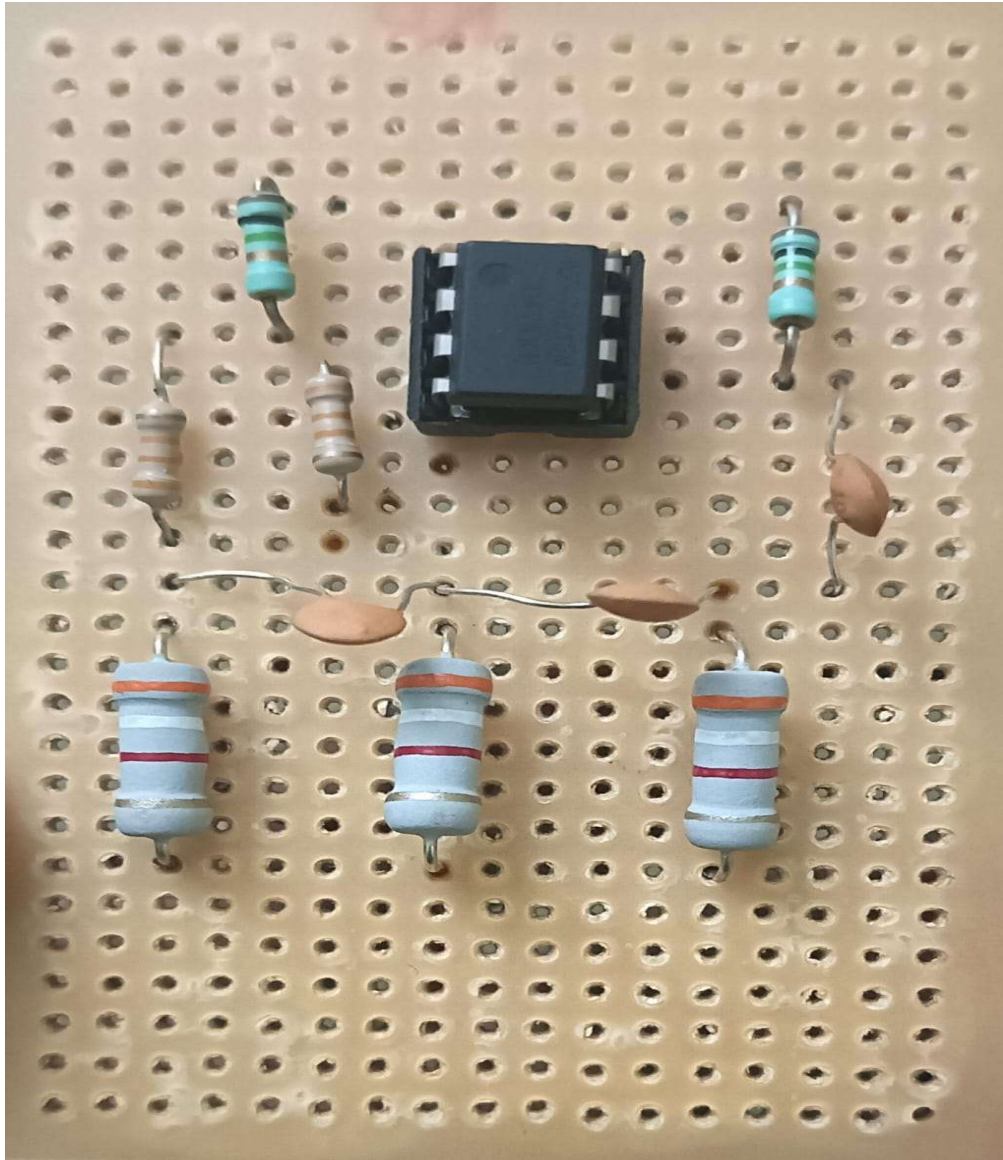





## OBSERVATIONS : OUTPUT (DIGITAL STORAGE OSCILLOSCOPE)




## OUTPUT + INPUT 1R (60 DEGREE SHIFT)

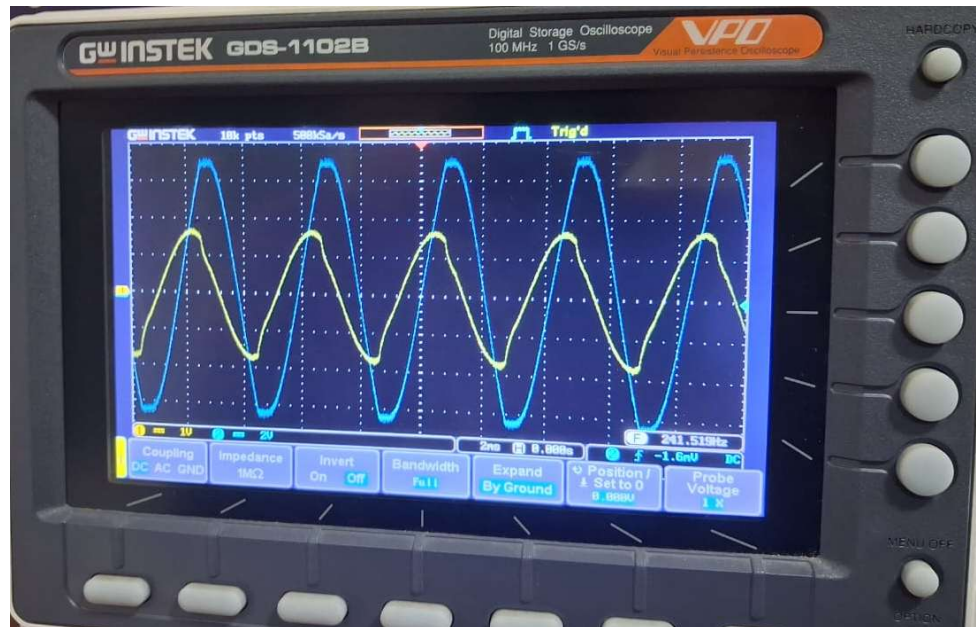

## OUTPUT + INPUT 2R (120 DEGREE SHIFT)

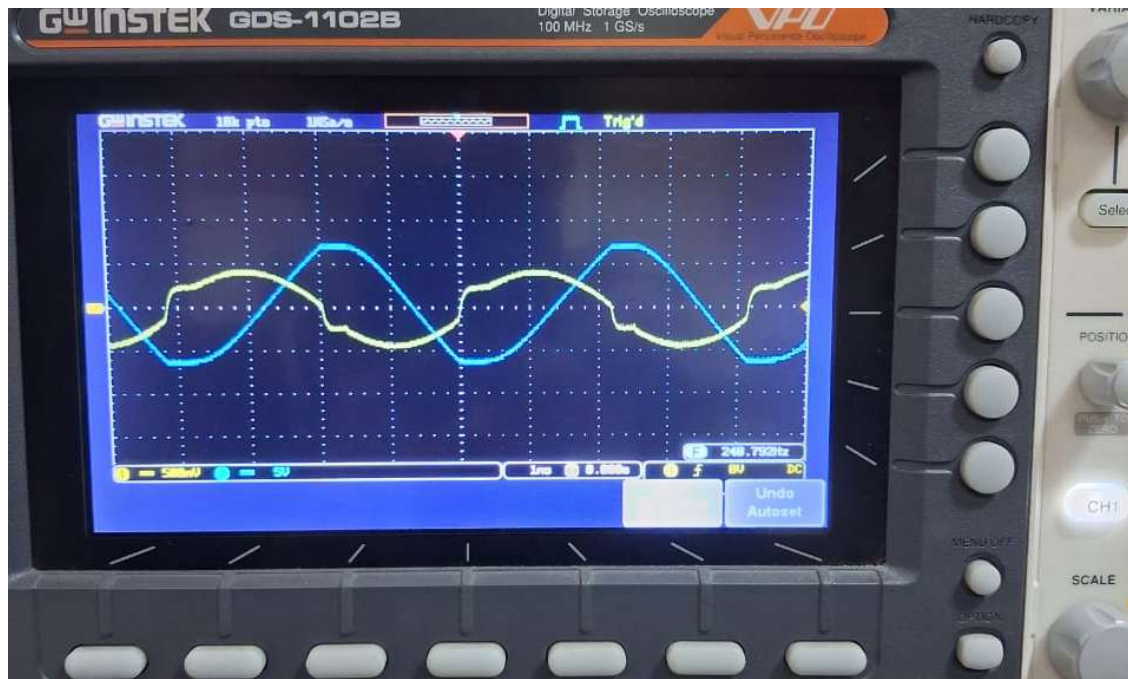

## OUTPUT + INPUT 3R (180 DEGREE SHIFT)

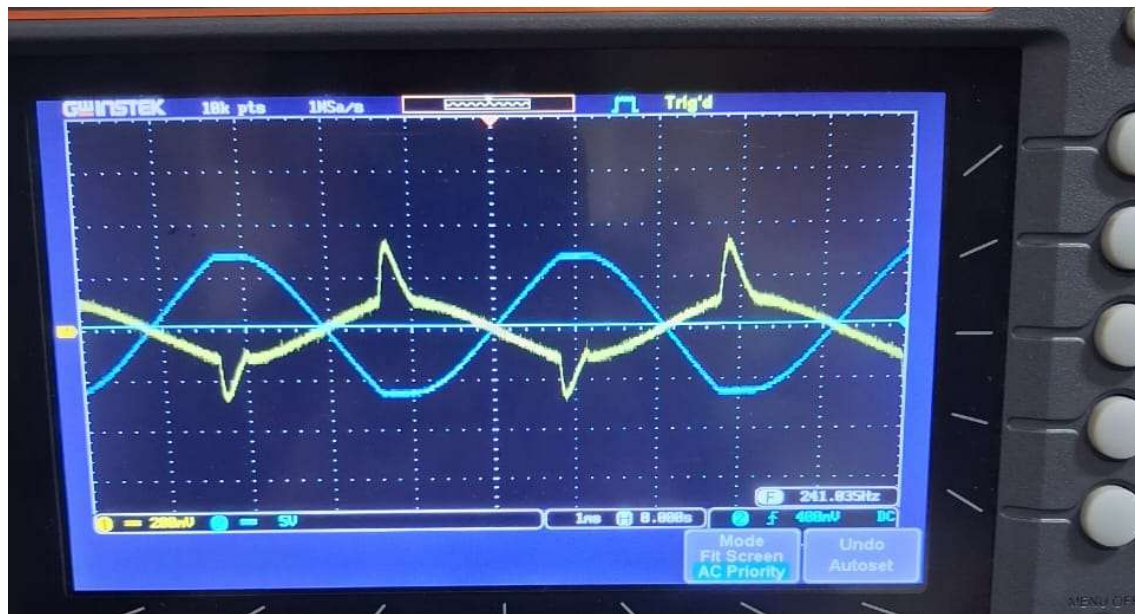

## CALCULATIONS:

### Gain:

$$A = \frac{R_f}{R_{in}} = \frac{2 \times 10^6}{33 \times 10^3} = 60.61$$

Formula for Frequency:

$$f = \frac{1}{2\pi RC\sqrt{6}}$$

Given Values:

- $R = 3.6 \text{ k}\Omega$
- $C = 0.1 \mu\text{F}$

Final Answer:

$$f = \frac{1}{2\pi \times 3.6 \times 10^3 \times 100 \times 10^{-9} \times \sqrt{6}} = 180.5 \text{ Hz}$$

**Gain of circuit : 60.61**

**Frequency of Oscillation : 180.5 Hz**



**Result:**

The RC Phase Shift Oscillator was successfully constructed using a 741 operational amplifier. The oscillator produced a stable sine wave at 180.5 Hz of frequency.

**Conclusion:**

The experiment verified that a 741 op-amp can be used to build a phase shift oscillator. By using three RC stages to provide a total phase shift of  $180^\circ$ , and combining it with the  $180^\circ$  phase shift of the inverting op-amp, the Barkhausen criterion for sustained oscillations was satisfied. The observed frequency of oscillation closely matched the theoretical value.

**Bibliography :**

1. Gaikwad Ramakant A.  
*Op-Amps and Linear Integrated Circuits.*

